

Examples (Simplification)

- $(A + AB) = A$
- $(A+B)(A+C) = A + BC$
- $(CAB)' + A' + AB)' = 0$
- $((AB+C)(\overline{AC}+BC)+ABC+\overline{AB})' = \overline{A(B+C)} \xrightarrow{\text{corrected}} AB$


AOI logic \rightarrow AND, OR, INVERTOR gates only circuit

NAND-NAND logic \rightarrow NAND gates only

NOR-NOR logic \rightarrow NOR gates only

- $X = A + BC + CD$

\Rightarrow AOI Logic Circuit

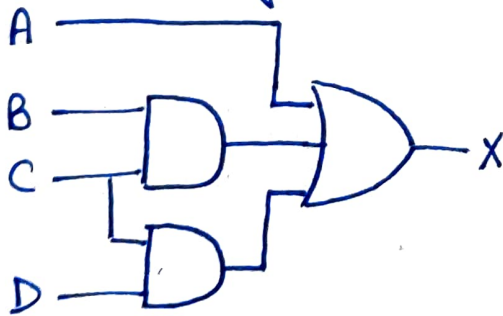

Converting into a
NAND-NAND logic

Placing bubbles

- Bubbled OR \sim NAND
- AND \rightarrow NAND


NAND-NAND to Inverter



Thus, final

NAND-NAND logic
(using only NAND gates)

$$X = A + BC + CD$$

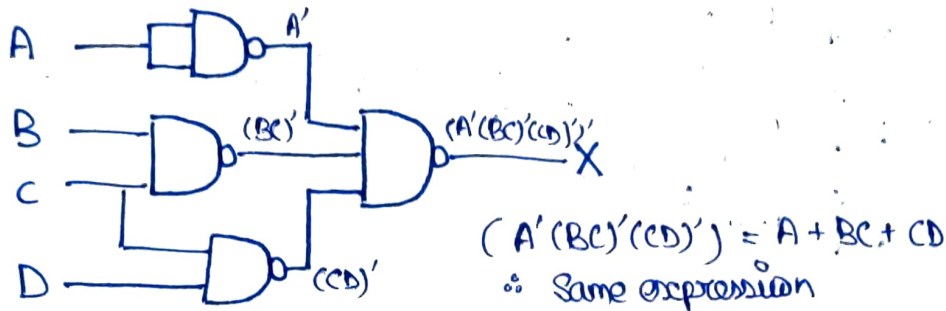

Same procedure for


NOR-NOR logic circuit

- ~~Placing Bubbles~~
- Place inverter for the extra bubble

Thus, Final


NOR-NOR logic

$$X = A + BC + CD$$

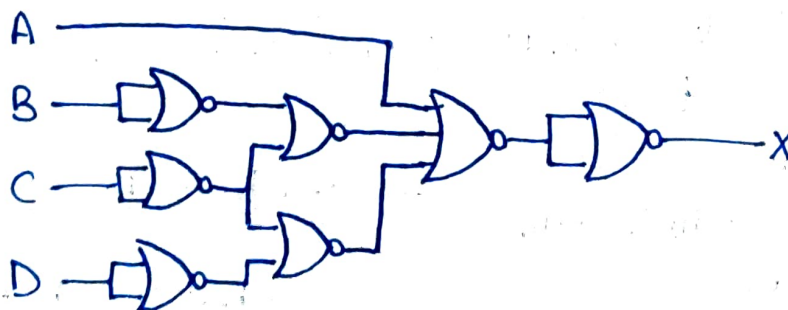


• $X = (A+B)(C+D)E$


AOI Logic Circuit

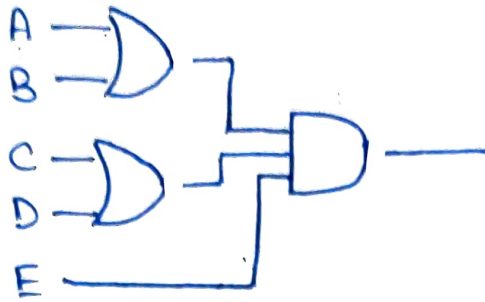

NAND-NAND Circuit

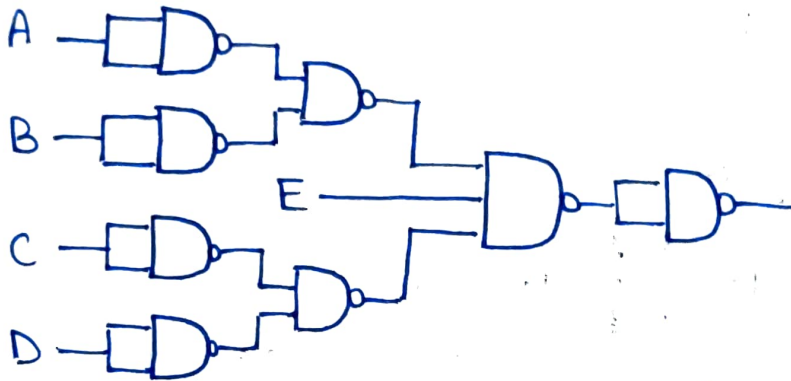

NOR-NOR Circuit

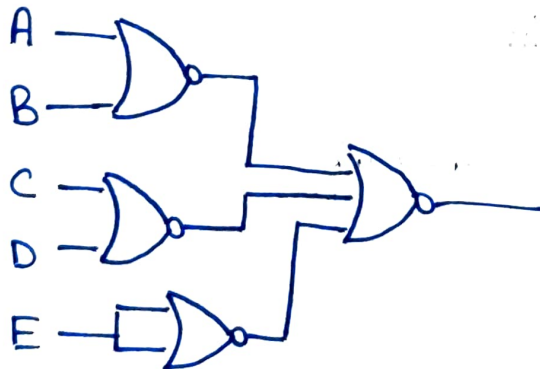

- A Reduced circuit is desired always
 \Rightarrow (Reduced circuit = Min no. of gates used)

For less complexity
time &
efficiency reasons

Two forms

\rightarrow SOP form

(Sum of Products form)

• $X = A + BC + CD$

\rightarrow POS form

(Sum Product of Sum form)

• $X = (A+B)(C+D)E$

SOP form

\Rightarrow Circuit Reduced \rightarrow ~~NOR-NOR~~ logic
NAND-NAND


POS form

\Rightarrow Circuit Reduced \rightarrow NOR-NOR logic


Eg Question,

1) $Y = A + BC + \bar{D}$

• AOI Logic

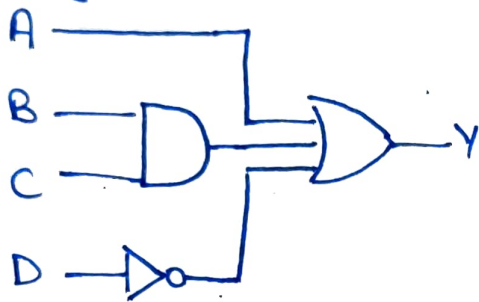

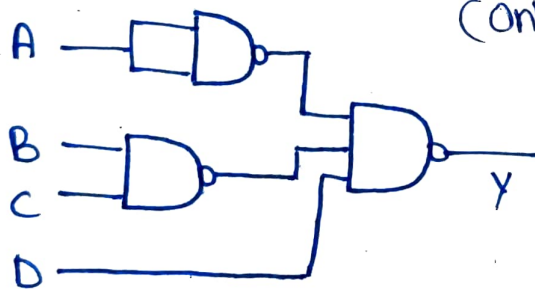
\Rightarrow NAND-NAND logic to be used, since SOP form



(Only 3 gates used)

NAND - 3 (better)
NOR - 6

2) $Y = (A' + B)(A' + D)(B + C')$

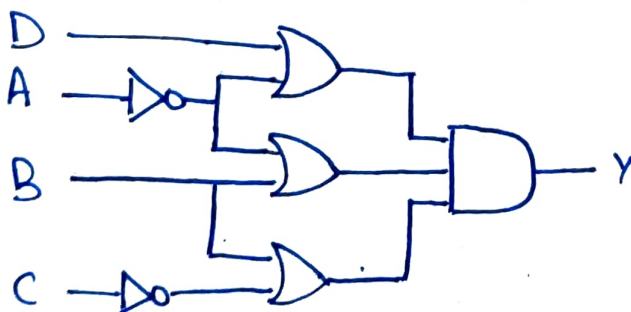


• AOI Logic

Since in POS form

\Rightarrow NOR-NOR logic to be used

NOR-NOR logic

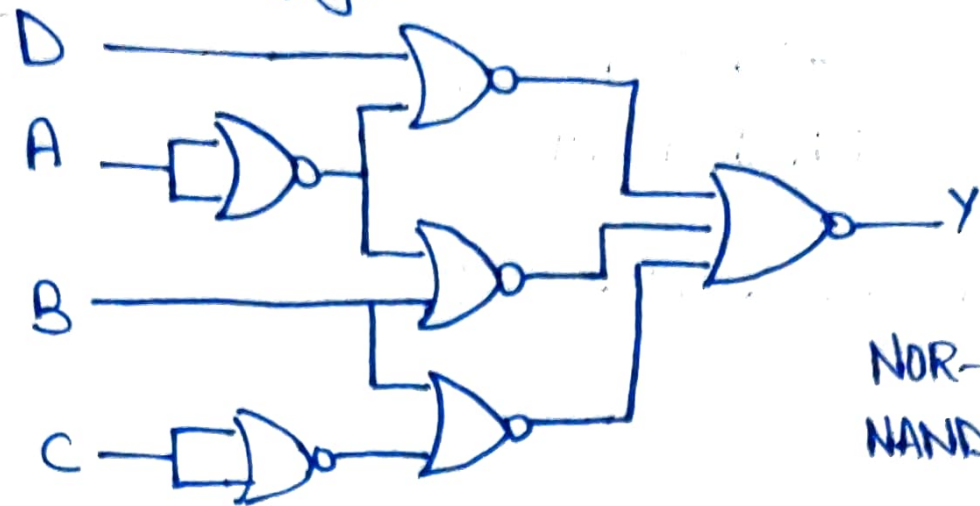

NOR-NOR \Rightarrow 6 (better)

NAND-NAND \Rightarrow 9

(Only 6 gates for NOR)