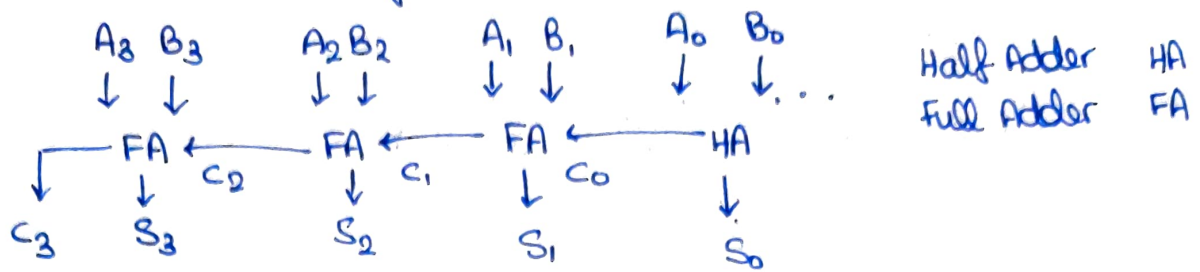


4 bit Parallel Binary Adder



Adding 4 one bit numbers

$$\begin{array}{r}
 A_3 \ A_2 \ A_1 \ A_0 \\
 + \ B_3 \ B_2 \ B_1 \ B_0 \\
 \hline
 C \ S_3 \ S_2 \ S_1 \ S_0
 \end{array}$$


⇒ Subtractions

Half Subtractor

Subtracts ^{one} 2 bits of variables

A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0
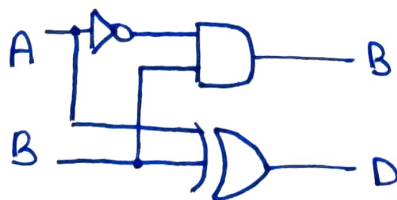
$$\begin{aligned}
 D &= A'B + AB' = A \oplus B = \cancel{A+B} \\
 B &= A'B
 \end{aligned}$$



Full Subtractor


Subtracts 3 one bit variables

A	B	C	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$$B = A'C + A'B AB' + BC'$$

$$D = A \oplus B \oplus C$$

4 bit Parallel Bit Subtractor

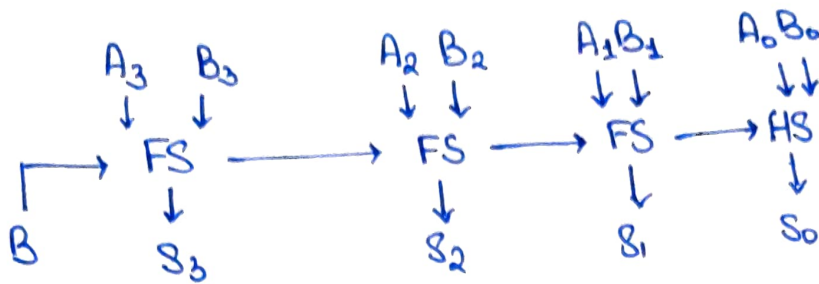

Parallel 4 Bit 1's complement Subtractor

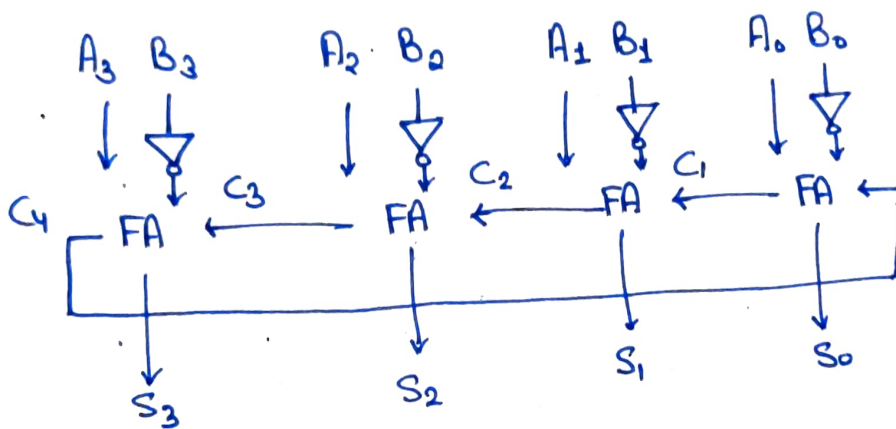

Eq. $1101 - 0110 = 0111$

1) we invert 0110 and add

$$\begin{array}{r} 1101 \\ + 1001 \\ \hline \end{array}$$

$$\begin{array}{r} 1101 \\ + 1001 \\ \hline 10110 \end{array}$$

2) we add back the carry

$$\begin{array}{r} 1001 \\ + 0110 \\ + 1 \\ \hline 0111 \end{array}$$


3) which was the original difference

If no carry is generated, then answer is in one's complement form and -ve

For final answer, invert the values
 $S_3 S_2 S_1 S_0 \rightarrow \overline{S_3} \overline{S_2} \overline{S_1} \overline{S_0}$

(Adding 1 to 2^0 's complement (complement))

2's Complement Adder/Subtractor

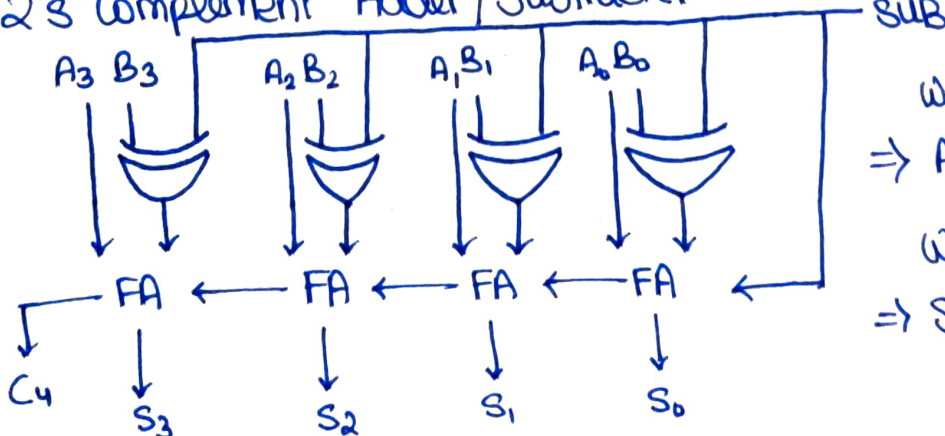

When SUB = 0
 \Rightarrow Adder Circuit

When SUB = 1
 \Rightarrow Subtractor Circuit