

# Digital Electronics

What is Electronics?

What is Digital Electronics?

## Digital Electronics

⇒ Digital Signal

- Not continuous
- Discrete values (finite)




Has two values

- lower value (lower potential)
- higher value (higher potential)

## Analog Electronics

⇒ Analog Signal

- Time varying
- Continuous nature

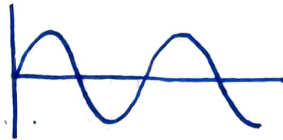

## Logic Gates


### NOT

x	y
0	1
1	0



### OR

a	b	y
0	0	0
0	1	1
1	0	1
1	1	1

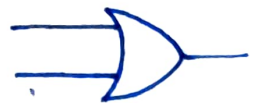

### AND

a	b	y
0	0	0
0	1	0
1	0	0
1	1	1



(multiplier)

$(AND)' \Rightarrow NAND$

$y'_{AND}$

1  
1  
1  
0



$(OR)' \Rightarrow NOR$

$y'_{OR}$

1  
0  
0  
0



Exclusive OR  $\Rightarrow$  XOR

a	b	y
0	0	0
0	1	1
1	0	1
1	1	0



(used for parity checking applications)

- if even 1s  $\Rightarrow$  low
- if odd 1s  $\Rightarrow$  high

Parties  $\rightarrow$  Odd = odd number of 1s  
Presence of 1s in any gate  $\rightarrow$  Even = even number of 1s

## De Morgan's Theorem

### Logical Fundamentals

$$\begin{aligned} A \cdot 0 &= 0 & A + 0 &= A \\ A \cdot 1 &= A & A + 1 &= 1 \\ A \cdot A &= A & A + A &= A \\ A \cdot \bar{A} &= 0 & A + \bar{A} &= 1 \end{aligned}$$

### Law of Complementation

$$\bar{0} = 1 \quad \bar{1} = 0$$

### Commutative Law

$$\begin{aligned} A + B &= B + A \\ AB &= BA \end{aligned}$$

### Associative Law

$$\begin{aligned} A + (B + C) &= (A + B) + C \\ A(BC) &= (AB)C \end{aligned}$$


Upon Applying These,

$$\Rightarrow \overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\Rightarrow \overline{A \cdot B} = \bar{A} + \bar{B}$$


"Complement of Sum is equal to AND of the complement of the inputs"  
...and vice versa

(NOR)  $\overline{A+B}$  =  $\overline{A} \cdot \overline{B}$  (Bubbled AND)



"to invert a signal  
place a bubble"

(NAND)  $\overline{A \cdot B}$  =  $\overline{A} + \overline{B}$  (Bubbled OR)



Examples (Simplification)

- $(A + AB) = A$
- $(A+B)(A+C) = A + BC$
- $((AB)' + A' + AB)' = 0$
- $(AB+C)(\overline{AC+BC}) + ABC + \overline{AB}Y = A(B+C)$

AOI logic  $\rightarrow$  AND, OR, INVERTOR gates only circuit

NAND-NAND logic  $\rightarrow$  NAND gates only

NOR-NOR logic  $\rightarrow$  NOR gates only